

15.4 The attractive forces exerted on the positive charge by the negative charges are shown in the sketch and have magnitudes


$$F_1 = F_2 = \frac{k_e q^2}{a^2} \quad \text{and} \quad F_3 = \frac{k_e q^2}{(a\sqrt{2})^2} = \frac{k_e q^2}{2a^2}$$

$$\Sigma F_x = F_2 + F_3 \cos 45^\circ = \frac{k_e q^2}{a^2} + \frac{k_e q^2}{2a^2} (0.707) = 1.35 \left(\frac{k_e q^2}{a^2} \right)$$

and
$$\Sigma F_y = F_1 + F_3 \sin 45^\circ = \frac{k_e q^2}{a^2} + \frac{k_e q^2}{2a^2} (0.707) = 1.35 \left(\frac{k_e q^2}{a^2} \right)$$

$$F_R = \sqrt{(\Sigma F_x)^2 + (\Sigma F_y)^2} = 1.91 \frac{k_e q^2}{a^2} \quad \text{and} \quad \theta = \tan^{-1} \left(\frac{\Sigma F_y}{\Sigma F_x} \right) = \tan^{-1}(1) = 45^\circ$$

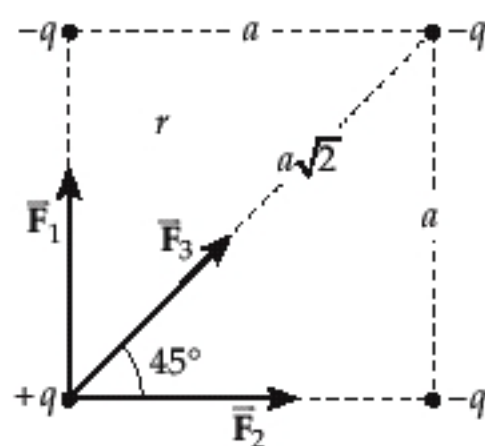so
$$\vec{F}_R = 1.91 \left(\frac{k_e q^2}{a^2} \right) \text{ along the diagonal toward the negative charge}$$



15.5 (a)
$$F = \frac{k_e (2e)^2}{r^2} = \left(8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \right) \frac{4(1.60 \times 10^{-19})^2}{(5.00 \times 10^{-15} \text{ m})^2} = \boxed{36.8 \text{ N}}$$

15.13 The forces on the $7.00 \mu\text{C}$ charge are shown at the right.

$$F_1 = \left(8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \right) \frac{(7.00 \times 10^{-6} \text{ C})(2.00 \times 10^{-6} \text{ C})}{(0.500 \text{ m})^2}$$

$$= 0.503 \text{ N}$$

$$F_2 = \left(8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \right) \frac{(7.00 \times 10^{-6} \text{ C})(4.00 \times 10^{-6} \text{ C})}{(0.500 \text{ m})^2}$$

$$= 1.01 \text{ N}$$


Thus, $\Sigma F_x = (F_1 + F_2) \cos 60.0^\circ = 0.755 \text{ N}$

and $\Sigma F_y = (F_1 - F_2) \sin 60.0^\circ = -0.436 \text{ N}$


The resultant force on the $7.00 \mu\text{C}$ charge is

$$F_R = \sqrt{(\Sigma F_x)^2 + (\Sigma F_y)^2} = 0.872 \text{ N at } \theta = \tan^{-1} \left(\frac{\Sigma F_y}{\Sigma F_x} \right) = -30.0^\circ$$

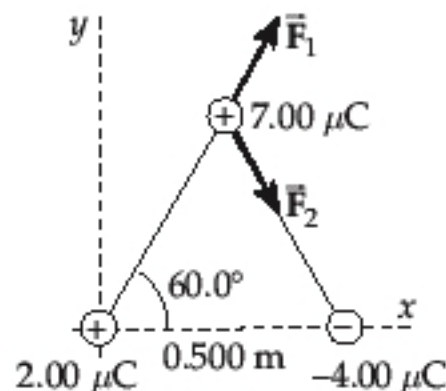or $\vec{F}_R = \boxed{0.872 \text{ N at } 30.0^\circ \text{ below the } +x \text{ axis}}$



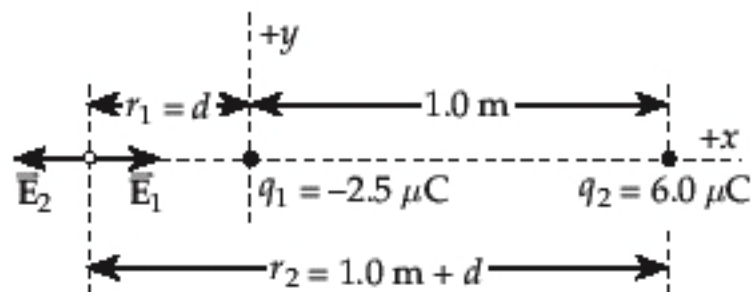15.27 If the resultant field is zero, the contributions from the two charges must be in opposite directions and also have equal magnitudes. Choose the line connecting the charges as the x -axis, with the origin at the $-2.5 \mu\text{C}$ charge. Then, the two contributions will have opposite directions only in the regions $x < 0$ and $x > 1.0 \text{ m}$. For the magnitudes to be equal, the point must be nearer the smaller charge. Thus, the point of zero resultant field is on the x -axis at $x < 0$.



Requiring equal magnitudes gives $\frac{k_e |q_1|}{r_1^2} = \frac{k_e |q_2|}{r_2^2}$ or $\frac{2.5 \mu\text{C}}{d^2} = \frac{6.0 \mu\text{C}}{(1.0 \text{ m} + d)^2}$

Thus, $(1.0 \text{ m} + d)\sqrt{\frac{2.5}{6.0}} = d$

Solving for d yields

$$d = 1.8 \text{ m}, \quad \text{or} \quad \boxed{1.8 \text{ m to the left of the } -2.5 \mu\text{C charge}}$$

16.13 (a) Calling the $2.00 \mu\text{C}$ charge q_3 ,


$$V = \sum_i \frac{k_e q_i}{r_i} = k_e \left(\frac{q_1}{r_1} + \frac{q_2}{r_2} + \frac{q_3}{\sqrt{r_1^2 + r_2^2}} \right)$$
$$= \left(8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \right) \left(\frac{8.00 \times 10^{-6} \text{ C}}{0.0600 \text{ m}} + \frac{4.00 \times 10^{-6} \text{ C}}{0.0300 \text{ m}} + \frac{2.00 \times 10^{-6} \text{ C}}{\sqrt{(0.0600)^2 + (0.0300)^2} \text{ m}} \right)$$

$$V = \boxed{2.67 \times 10^6 \text{ V}}$$

(b) Replacing $2.00 \times 10^{-6} \text{ C}$ by $-2.00 \times 10^{-6} \text{ C}$ in part (a) yields

$$V = \boxed{2.13 \times 10^6 \text{ V}}$$

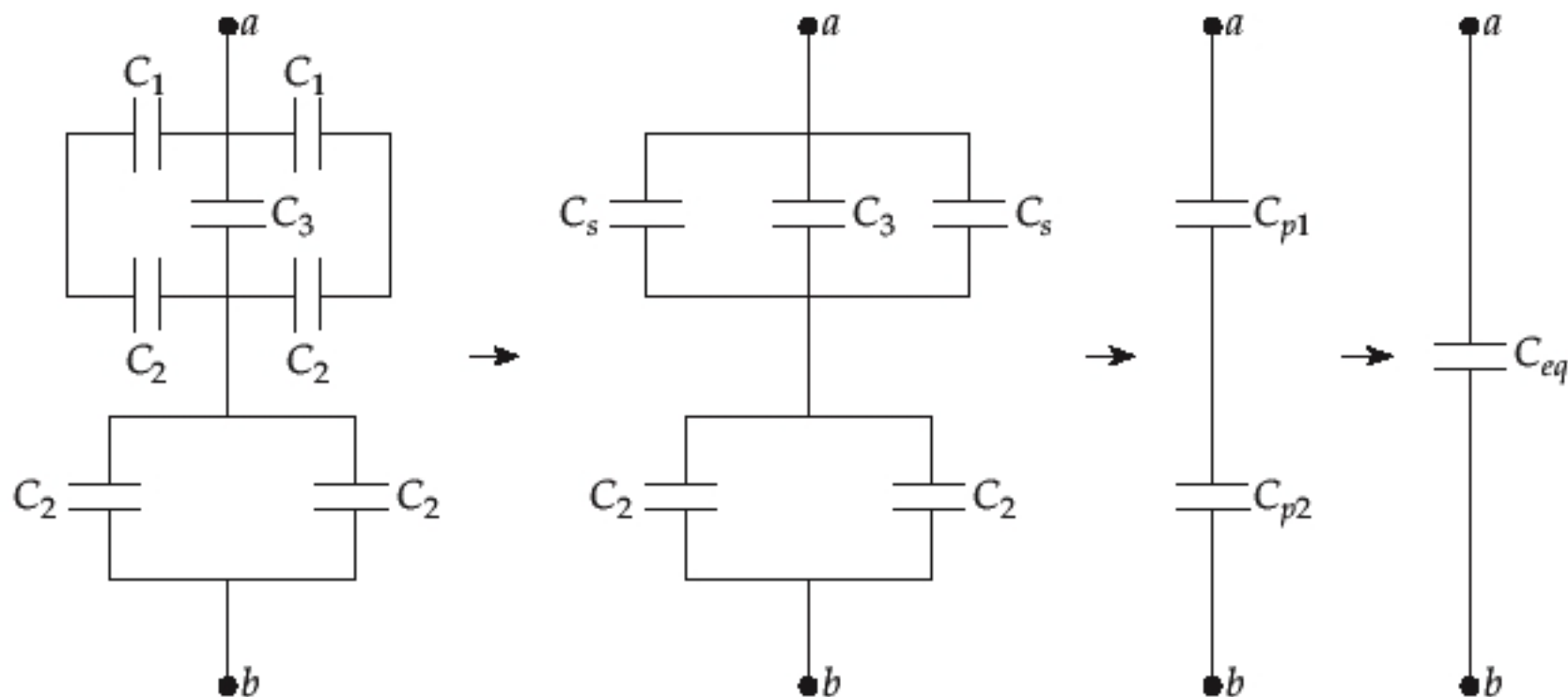16.40 The original circuit reduces to a single equivalent capacitor in the steps shown below.



$$C_s = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \left(\frac{1}{5.00 \mu\text{F}} + \frac{1}{10.0 \mu\text{F}} \right)^{-1} = 3.33 \mu\text{F}$$

$$C_{p1} = C_s + C_3 + C_s = 2(3.33 \mu\text{F}) + 2.00 \mu\text{F} = 8.66 \mu\text{F}$$

$$C_{p2} = C_2 + C_2 = 2(10.0 \mu\text{F}) = 20.0 \mu\text{F}$$

$$C_{eq} = \left(\frac{1}{C_{p1}} + \frac{1}{C_{p2}} \right)^{-1} = \left(\frac{1}{8.66 \mu\text{F}} + \frac{1}{20.0 \mu\text{F}} \right)^{-1} = \boxed{6.04 \mu\text{F}}$$

16.43 The capacitance is

$$C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(2.00 \times 10^{-4} \text{ m}^2)}{5.00 \times 10^{-3} \text{ m}} = 3.54 \times 10^{-13} \text{ F}$$

and the stored energy is

$$W = \frac{1}{2}C(\Delta V)^2 = \frac{1}{2}(3.54 \times 10^{-13} \text{ F})(12.0 \text{ V})^2 = \boxed{2.55 \times 10^{-11} \text{ J}}$$

16.47 The initial capacitance (with air between the plates) is $C_i = Q/(\Delta V)_i$, and the final capacitance (with the dielectric inserted) is $C_f = Q/(\Delta V)_f$ where Q is the constant quantity of charge stored on the plates.

Thus, the dielectric constant is $\kappa = \frac{C_f}{C_i} = \frac{(\Delta V)_i}{(\Delta V)_f} = \frac{100 \text{ V}}{25 \text{ V}} = \boxed{4.0}$

17.4 $\Delta Q = I(\Delta t)$ and the number of electrons is

$$n = \frac{\Delta Q}{|e|} = \frac{I(\Delta t)}{|e|} = \frac{(60.0 \times 10^{-6} \text{ C/s})(1.00 \text{ s})}{1.60 \times 10^{-19} \text{ C}} = \boxed{3.75 \times 10^{14} \text{ electrons}}$$

17.13 From $R = \frac{\rho L}{A}$, we obtain $A = \frac{\pi d^2}{4} = \frac{\rho L}{R}$, or

$$d = \sqrt{\frac{4\rho L}{\pi R}} = \sqrt{\frac{4(5.6 \times 10^{-8} \Omega \cdot \text{m})(2.0 \times 10^{-2} \text{ m})}{\pi(0.050 \Omega)}} = 1.7 \times 10^{-4} \text{ m} = \boxed{0.17 \text{ mm}}$$

17.52 The resistance of the 4.0 cm length of wire between the feet is

$$R = \frac{\rho L}{A} = \frac{(1.7 \times 10^{-8} \Omega \cdot \text{m})(0.040 \text{ m})}{\pi(0.011 \text{ m})^2} = 1.79 \times 10^{-6} \Omega,$$

so the potential difference is

$$\Delta V = IR = (50 \text{ A})(1.79 \times 10^{-6} \Omega) = 8.9 \times 10^{-5} \text{ V} = \boxed{89 \mu\text{V}}$$

17.57 The current in the wire is $I = \frac{\Delta V}{R} = \frac{15.0 \text{ V}}{0.100 \Omega} = 150 \text{ A}$

Then, from $v_d = I/nqA$, the density of free electrons is

$$n = \frac{I}{v_d e (\pi r^2)} = \frac{150 \text{ A}}{(3.17 \times 10^{-4} \text{ m/s})(1.60 \times 10^{-19} \text{ C})\pi(5.00 \times 10^{-3} \text{ m})^2}$$

or $n = \boxed{3.77 \times 10^{28} / \text{m}^3}$

- 18.8 (a) The rules for combining resistors in series and parallel are used to reduce the circuit to an equivalent resistor in the stages shown below. The result is $R_{eq} = \boxed{5.13 \Omega}$.

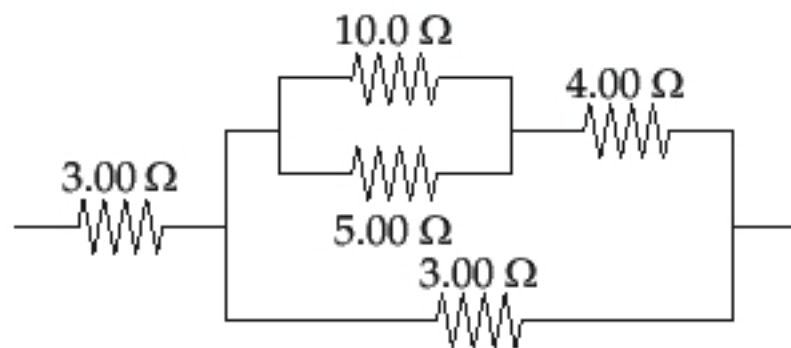


Figure 1

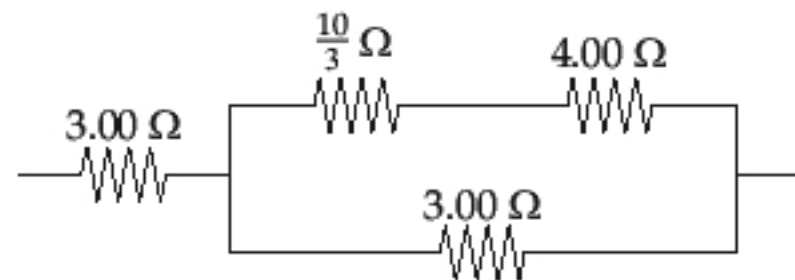


Figure 2

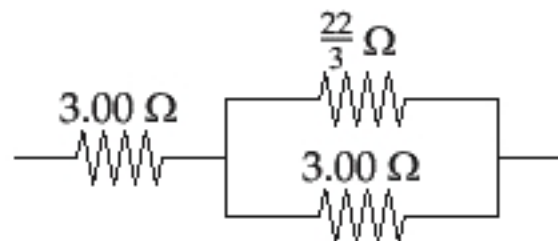


Figure 3

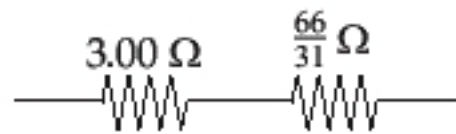


Figure 4

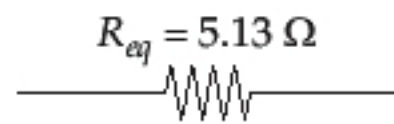


Figure 5

18.16 Going counterclockwise around the upper loop, applying Kirchhoff's loop rule, gives

$$+15.0 \text{ V} - (7.00)I_1 - (5.00)(2.00 \text{ A}) = 0$$

or
$$I_1 = \frac{15.0 \text{ V} - 10.0 \text{ V}}{7.00 \Omega} = \boxed{0.714 \text{ A}}$$


From Kirchhoff's junction rule, $I_1 + I_2 - 2.00 \text{ A} = 0$

so
$$I_2 = 2.00 \text{ A} - I_1 = 2.00 \text{ A} - 0.714 \text{ A} = \boxed{1.29 \text{ A}}$$

Going around the lower loop in a clockwise direction gives

$$+\mathcal{E} - (2.00)I_2 - (5.00)(2.00 \text{ A}) = 0$$

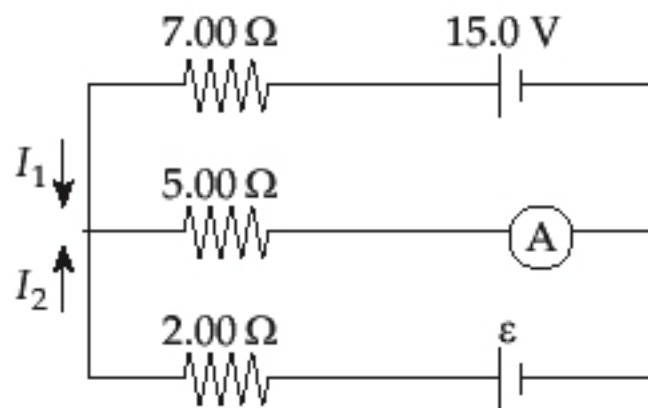or
$$\mathcal{E} = (2.00 \Omega)(1.29 \text{ A}) + (5.00 \Omega)(2.00 \text{ A}) = \boxed{12.6 \text{ V}}$$



18.27 Assume currents I_1 , I_2 , and I_3 in the directions shown. Then, using Kirchhoff's junction rule at junction a gives

$$I_3 = I_1 + I_2 \quad (1)$$

Applying Kirchhoff's loop rule on the upper loop,

$$+20.0 \text{ V} - (30.0)I_1 + (5.00)I_2 - 10.0 \text{ V} = 0$$

$$\text{or} \quad 6I_1 - I_2 = 2.00 \text{ A} \quad (2)$$

and for the lower loop, $+10.0 \text{ V} - (5.00)I_2 - (20.0)I_3 = 0$

$$\text{or} \quad I_2 + 4I_3 = 2.00 \text{ A} \quad (3)$$

Solving equations (1), (2), and (3) simultaneously yields

$$\boxed{I_1 = 0.353 \text{ A}, I_2 = 0.118 \text{ A}, \text{ and } I_3 = 0.471 \text{ A}}$$

